 


Lab 4

Prelab

1)



$\overline{SET} - SET_- = 0$, out(Q) high

SET-	RESET-	Q	$Q^+ = Q(n+1)$
Low (Q forced high)	Low (Q forced low)		Unknown
High (Q forced low)	High (Q forced high)		Q (unchanged)

- gated S-R Latch reduces sensitivity of outputs to changing inputs
clock signal must be high for S-R latch to respond to input signals
- Latch should change only once for each application of the clock
- Main secondary flip flops are a variation of the two phase clock approach for outputs from latches controlled by one phase of clock or another by the other phase of the clock.


- S-R latches improve our rejection of glitches on the inputs, but suffer from drawbacks
 - S-R is sensitive to glitches
 - D-type latch is either transparent (output follows input) or latched (output is held at the last value input)
 - D-type latch makes sure with an inverter that the inputs S & R they guaranteed to not be asserted at the same time, eliminating any invalid inputs
- (half clock)
gate cycle
high

• Flip-Flops [D-type]

② a) Should S & R signals be allowed to change while clock (G) is high?

Since this is a gated S-R Latch, it tends to be less sensitive with the effect changing inputs has on the output. Since clock signal is high the changing S & R signals are allowed to change which the S-R latch responds to those input signals.

b) For a gated S-R latch

 

Input:

SET $\xrightarrow{\text{PIN } 1}$ GREEN

RESET $\xrightarrow{\text{PIN } 2}$ RED

clock $\xrightarrow{\text{PIN } 3}$ Yellow

output:

Q $\xrightarrow{\text{PIN } 1}$ Purple

Q' $\xrightarrow{\text{PIN } 2}$ orange

Read Lap 1b

bin.

bit files