

Name: Danyal Falsafi

Section: 002

X500: falsa003

### Lab 5a: State-Machines

#### 1. K - Maps and Equations

Next A k-map  $\Sigma m(0,1,2,4,5,6)$

	A	0	1
B \ C	0	1	0
0	0	1	1
1	1	0	0
0	1	1	0
1	0	1	0

Handwritten K-map diagram showing two groups:

- A group of four cells (00, 01, 10, 11) in the first column (A=0) is circled and labeled  $\bar{B}$ .
- A group of four cells (00, 10, 01, 11) in the second column (A=1) is circled and labeled  $\bar{C}$ .


Handwritten equation:

$$F_{NA} = \bar{B} + \bar{C}$$

K- Map and Equation for NA




Next B k-map  $\Sigma m(4,5,6,7)$

 

K- Map and Equation for NB



Next C k-map  $\Sigma m(2,3,6,7)$

 


$$F_{NC} = B$$

K- Map and Equation for NC

## 2. Schematic for State-Transition



Schematic

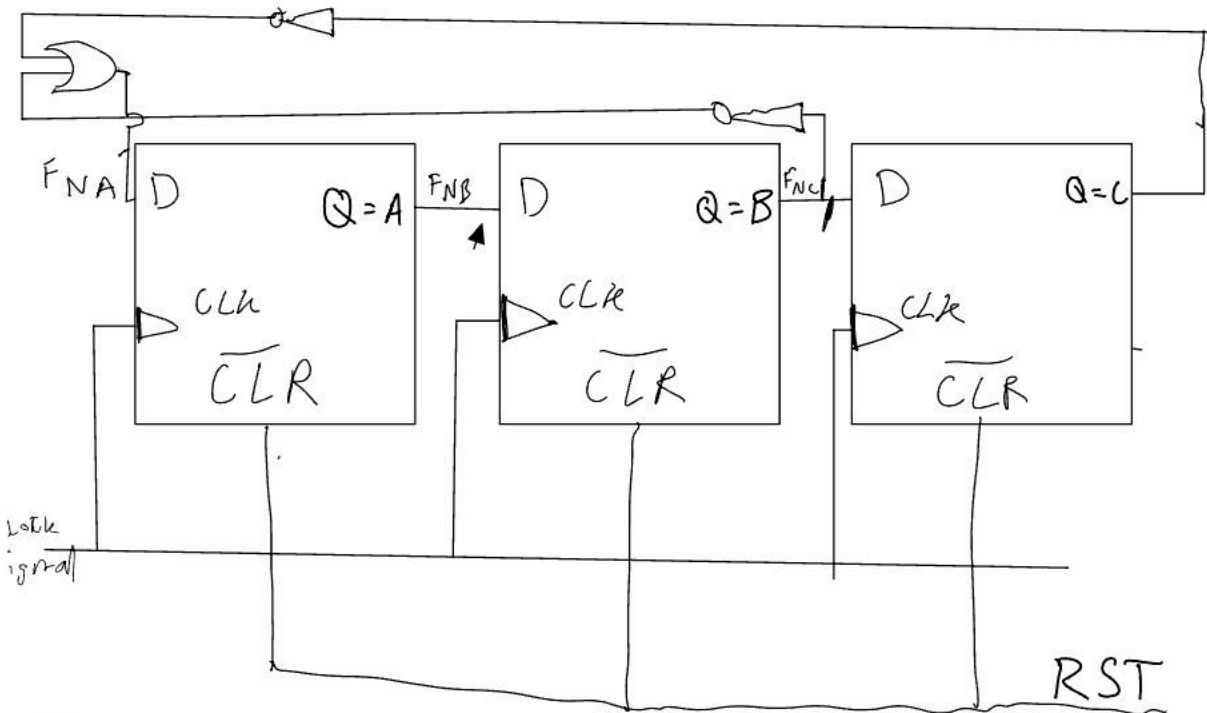

$F_{NC} = \text{Next} + C$  ;  $F_{NA} = \text{Next} + A$  ;  $F_{NB} = \text{Next} + B$

**Schematic for the State-Transitions on Paper (NOT the State-Transition Diagram)**  
**(Complete this on Paper)**

### 3. Verilog Code for State-Machine

## DFF.v:

```
module DFF(  
    output Q,  
    input D,  
    input NRST,  
    input CLK  
);  
  
    reg Q;  
  
    always @(posedge CLK, negedge NRST)  
    begin  
        if (~NRST)  
            Q <= 1'b0;  
        else  
            Q <= D;  
        end  
    endmodule
```

## Lab5\_Schem.v:

```
module Lab5_Schem(  
    output A,  
    output B,  
    output C,  
    input RESET,  
    input CLK  
);  
  
    wire NextA, NextB, NextC;  
  
    assign NextA = (~B) | (~C);
```


```
assign NextB = A;
assign NextC = B;
```

```
DFF FA0(A, NextA, ~RESET, CLK);
DFF FA1(B, NextB, ~RESET, CLK);
DFF FA2(C, NextC, ~RESET, CLK);
```

```
endmodule
```

Copy of Verilog Code

#### 4. Schematic from Vivado

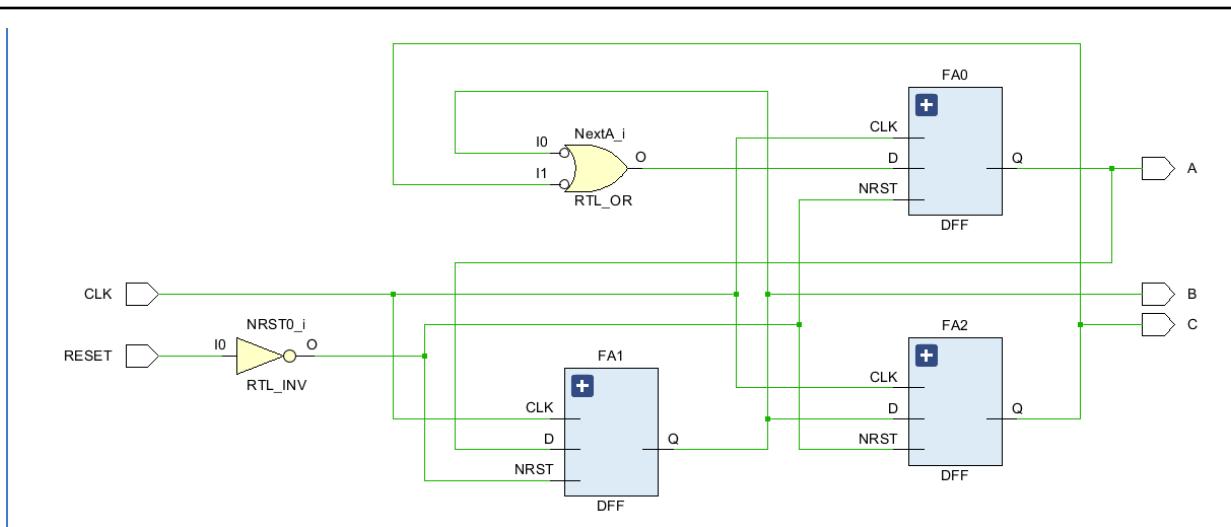

The only difference is that the RESET is inverted since in the D Flip Flop module the input NRST was inverted to become a regular RESET input. As a result the NRST is playing its part for the DFF module when the RESET is inverted proving that both the schematic on Vivado is the exact same as the schematic drawn in the prelab.

\*Note the OR gate has both its inputs (NextC and NextB) inverted

Schematic for Asynchronous/Synchronous Reset **obtained after Elaboration of Verilog Design.**

**If this matches the schematic on paper, you are awarded 10pts.**

**Else**

**Explain why there is a mismatch? (This gets you full points)**

## 5. Testbench

```
module Lab5_TB (  
    // list your ports here if any  
);  
  
reg Reset, Clock;  
wire NA,NB,NC;  
  
Lab5_Schem inst (  
    .RESET(Reset),  
    .CLK(Clock),  
    .A(NA),  
    .B(NB),  
    .C(NC)  
);  
  
initial  
begin  
    Clock = 0;  
    Reset = 1;  
    #25  
    Reset = 0;  
    #25  
  
    Clock = 1;  
    #50  
    Clock = 0;  
    #50  
    Clock = 1;  
    #50
```

```
Clock = 0;
#50
Clock = 1;
#50
Clock = 0;
#50
Clock = 1;
#50
Clock = 0;
#50
Clock = 1;
#50
Clock = 0;
#50
Clock = 1;
#50
Clock = 0;
#50
Clock = 1;
#50
Clock = 0;
#50
Clock = 1;
#50
Clock = 0;
#50
Clock = 1;
#50
Clock = 0;


end

endmodule
```

Copy of Testbench used for Simulation



## 6. Simulated Waveform

 

Screenshot of Waveforms after Behavioral Simulation

## 7. Constraint File

```
set_property PACKAGE_PIN V17 [get_ports {CLK}]
set_property IOSTANDARD LVCMOS33 [get_ports {CLK}]
set_property PACKAGE_PIN V16 [get_ports {RESET}]
set_property IOSTANDARD LVCMOS33 [get_ports {RESET}]

set_property CLOCK_DEDICATED_ROUTE FALSE [get_nets {CLK_IBUF}]
set_property CLOCK_DEDICATED_ROUTE FALSE [get_nets {CLK_IBUF_BUFG}]

## LEDs
set_property PACKAGE_PIN U16 [get_ports {A}]
set_property IOSTANDARD LVCMOS33 [get_ports {A}]
set_property PACKAGE_PIN E19 [get_ports {B}]
set_property IOSTANDARD LVCMOS33 [get_ports {B}]
set_property PACKAGE_PIN U19 [get_ports {C}]
set_property IOSTANDARD LVCMOS33 [get_ports {C}]
```

Copy of Constraint File used for Implementation

**Lab 5b: Bi-Directional Shift Register**


## 1. Verilog Code for State-Machine

```
`timescale 1ns / 1ps
```

```
module Lab5BFinal(  
    input [7:0] inputNumber,  
    input RightNotLeft,  
    input [2:0]N,  
    input reset,  
    input clk,  
    output [7:0] OutputNumber  
);  
    reg [7:0]OutputNumber;  
  
    always @(posedge clk or posedge reset)  
    begin  
        if (reset) begin  
            OutputNumber <= 8'b0;  
        end  
        else begin  
            if(RightNotLeft)  
                OutputNumber <= (inputNumber>>N) | (inputNumber<<(8-N));  
            else  
                OutputNumber <=( inputNumber << N )| ( inputNumber >>(8-N));  
            end  
        end  
    end  
  
endmodule
```

Copy of Verilog Code with Asynchronous Reset Low

## 2. Schematic from Vivado

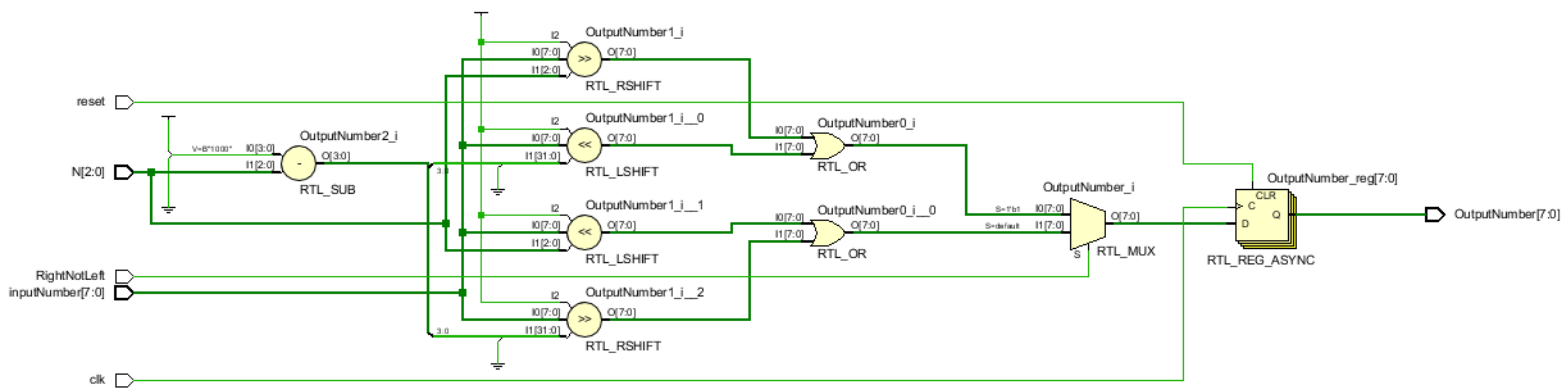

Schematic of Bi-directional Shift Register with Asynchronous Reset **obtained after Elaboration of Verilog Design.**

## 3. Testbench

```
`timescale 1ns / 1ps
```

```
module Lab5bfinal_tb(
```

```
    );  
    reg clk = 0;  
    reg RightNotLeft;  
    reg[7:0] inputNumber;  
    reg reset=0;  
    reg [2:0] N;  
    wire [7:0]OutputNumber;
```

```
    Lab5BFinal inst(  
        .inputNumber(inputNumber),  
        .clk(clk),  
        .reset(reset),  
        .RightNotLeft(RightNotLeft),  
        .N(N),  
        .OutputNumber(OutputNumber)  
    );
```

```
    always #10 begin
```

```
        clk<=~clk;
```

```
    end
```

```
    initial
```

```
    begin
```

```
        inputNumber = 8'b00000000; N = 3'd0; RightNotLeft = 0;reset = 1;
```

```
        #40
```

```
        inputNumber=8'b11001100; RightNotLeft=1; N=3'd2;reset=0;
```

```
        #40
```

```
        inputNumber = 8'b10101010; RightNotLeft = 0; N = 3'd1;reset = 0;
```

```
        #40
```

```
        inputNumber =8'b11100000; RightNotLeft=1; N=3'd5; reset = 0;
```

```
        #40
```

```
        inputNumber = 8'b00000001; RightNotLeft = 0; N = 3'd7; reset = 0;
```

```
        #40
```


```
        inputNumber = 8'b01010101; RightNotLeft = 1; N = 3'd1;reset = 1;
```

```
    end
```

endmodule

Copy of Testbench used for Simulation

#### 4. Simulated Waveform

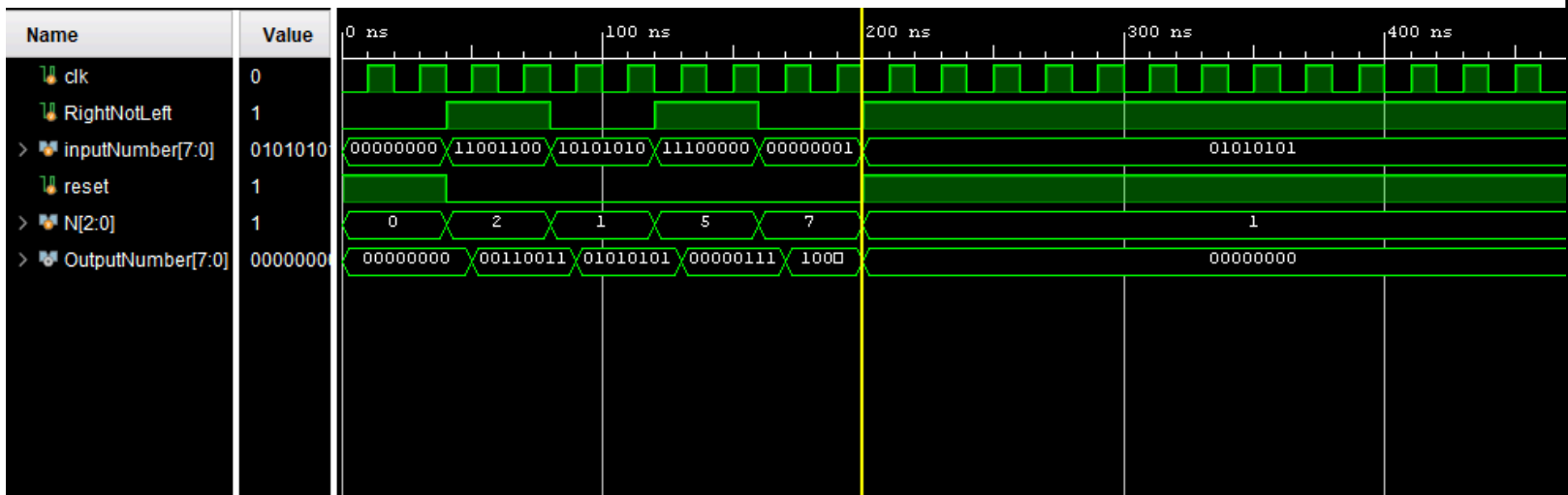

Screenshot of Waveforms after Behavioral Simulation

## 5. Constraint File

## ## Switches

```
set_property PACKAGE_PIN V17 [get_ports {inputNumber[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {inputNumber[0]}]
set_property PACKAGE_PIN V16 [get_ports {inputNumber[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {inputNumber[1]}]
set_property PACKAGE_PIN W16 [get_ports {inputNumber[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {inputNumber[2]}]
set_property PACKAGE_PIN W17 [get_ports {inputNumber[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {inputNumber[3]}]
set_property PACKAGE_PIN W15 [get_ports {inputNumber[4]}]
set_property IOSTANDARD LVCMOS33 [get_ports {inputNumber[4]}]
set_property PACKAGE_PIN V15 [get_ports {inputNumber[5]}]
set_property IOSTANDARD LVCMOS33 [get_ports {inputNumber[5]}]
set_property PACKAGE_PIN W14 [get_ports {inputNumber[6]}]
set_property IOSTANDARD LVCMOS33 [get_ports {inputNumber[6]}]
set_property PACKAGE_PIN W13 [get_ports {inputNumber[7]}]
set_property IOSTANDARD LVCMOS33 [get_ports {inputNumber[7]}]
set_property PACKAGE_PIN T2 [get_ports {N[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {N[0]}]
set_property PACKAGE_PIN R3 [get_ports {N[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {N[1]}]
set_property PACKAGE_PIN W2 [get_ports {N[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {N[2]}]
set_property PACKAGE_PIN U1 [get_ports {clk}]
    set_property IOSTANDARD LVCMOS33 [get_ports {clk}]
set_property PACKAGE_PIN T1 [get_ports {RightNotLeft}]
set_property IOSTANDARD LVCMOS33 [get_ports {RightNotLeft}]
set_property PACKAGE_PIN R2 [get_ports {reset}]
set_property IOSTANDARD LVCMOS33 [get_ports {reset}]
```

## ## LEDs

```
set_property PACKAGE_PIN U16 [get_ports {OutputNumber[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {OutputNumber[0]}]
set_property PACKAGE_PIN E19 [get_ports {OutputNumber[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {OutputNumber[1]}]
set_property PACKAGE_PIN U19 [get_ports {OutputNumber[2]}]
```



```
set_property IOSTANDARD LVCMOS33 [get_ports {OutputNumber[2]}]
set_property PACKAGE_PIN V19 [get_ports {OutputNumber[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {OutputNumber[3]}]
set_property PACKAGE_PIN W18 [get_ports {OutputNumber[4]}]
set_property IOSTANDARD LVCMOS33 [get_ports {OutputNumber[4]}]
set_property PACKAGE_PIN U15 [get_ports {OutputNumber[5]}]
set_property IOSTANDARD LVCMOS33 [get_ports {OutputNumber[5]}]
set_property PACKAGE_PIN U14 [get_ports {OutputNumber[6]}]
set_property IOSTANDARD LVCMOS33 [get_ports {OutputNumber[6]}]
set_property PACKAGE_PIN V14 [get_ports {OutputNumber[7]}]
set_property IOSTANDARD LVCMOS33 [get_ports {OutputNumber[7]}]
```

#Clock Signal every 10ns

```
#create_clock -period 10.000 -name sys_clk_pin -waveform {0.000 5.000} -add [get_ports clk]
set_property CLOCK_DEDICATED_ROUTE FALSE [get_nets {clk_IBUF}]
set_property CLOCK_DEDICATED_ROUTE FALSE [get_nets {clk_IBUF_BUFG}]
```

Copy of Constraint File used for Implementation